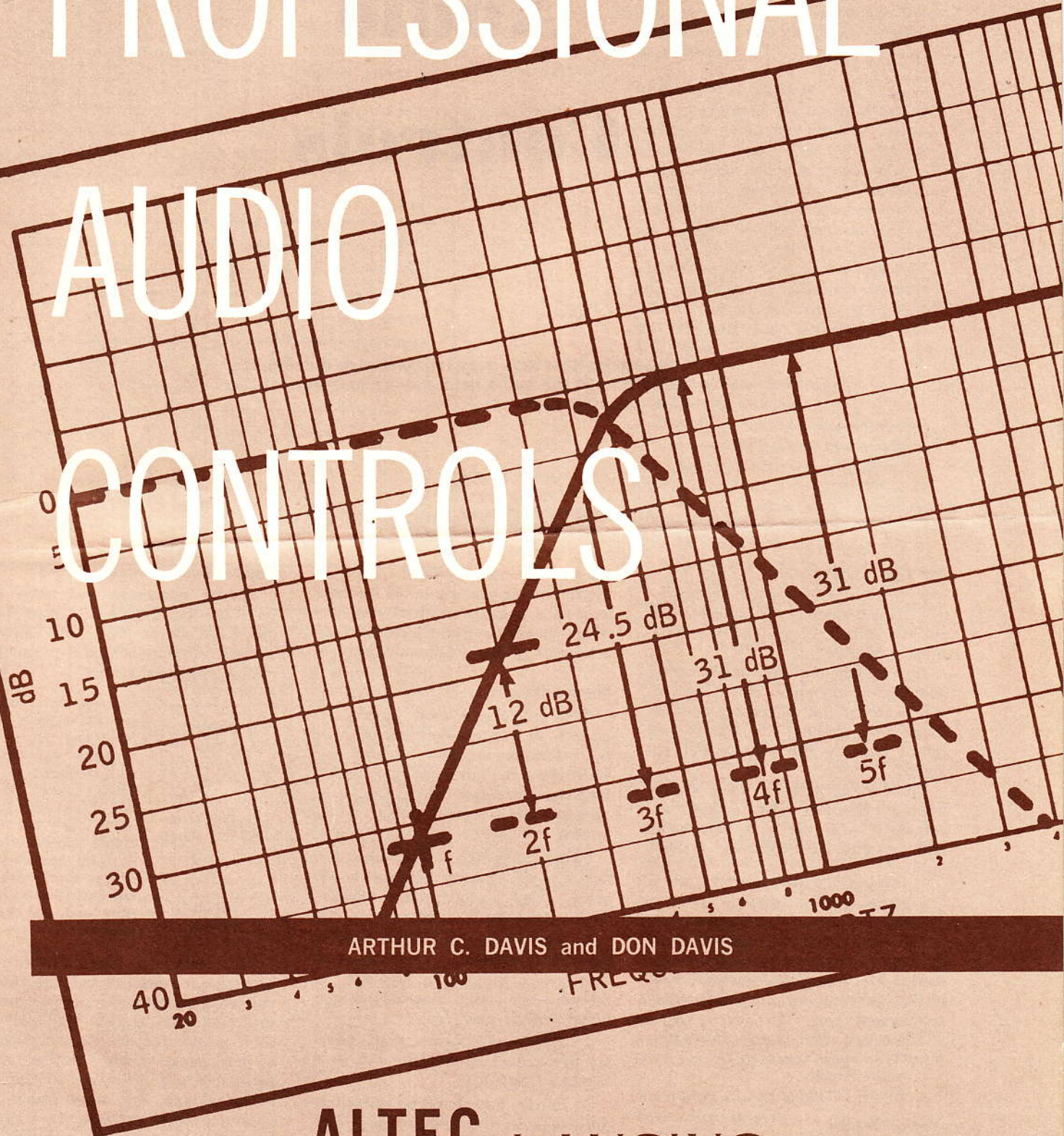


PROFESSIONAL

AUDIO

CONTROLS



ARTHUR C. DAVIS and DON DAVIS

ALTEC LANSING

Professional Audio Controls

The authors have long been recognized as outstanding authorities in the audio field and are members of the Altec Lansing staff.

ARTHUR C. DAVIS and DON DAVIS

THE PROFESSIONAL AUDIO ENGINEER has long used fixed-gain/passive-control components in recording, broadcasting, and reinforcement system design.

Increasingly, the audio experimenter and high-quality-audio buff is becoming aware of the differences between home high fidelity components and those used by the professional engineer.

Three major differences are obvious when professional audio systems are compared with the very best home hi-fi systems. Professional systems utilize:

1. Fixed gain amplifiers.
2. Passive control devices.
3. Low impedance transmission circuits.

Not so immediately apparent are the factors of greater precision, longer service life, and greater versatility of service inherent in the professional components.

There are two types of controls possible in audio systems:

1. Active circuits.
2. Passive circuits.

Active Circuits

Active circuits are those that exert the required control by means of varying changes in the feedback circuit of an amplifier. Usually such controls

are basically some form of frequency-discriminating network in the feedback loop of a negative-feedback amplifier which shapes the gain-frequency characteristics of the total amplifier.

Passive Circuits

This article is a short general discussion of the passive controls used in professional audio systems and shows how the advanced high fidelity buff can graduate to a fixed-gain, passive-control, professional sound system.

Passive controls are those that exert the desired change without power being added in the process. Passive devices take the form of:

1. *Attenuators.* Normally a resistive network that attenuates equally at all frequencies within the bandpass of interest while maintaining constant terminal impedances.

2. *Equalizers.* Devices that attenuate or restore inserted attenuation at selected frequencies.

3. *Filters.* Filters and special effects devices under this category are high- and low-pass filters and notch filters. These devices are characterized by zero insertion loss at all frequencies other than their operating frequencies.

Passive Equalizers and Filters

Passive equalizers and filters can be of the RC, LC, or RLC type. They can be constant "K," "M" derived, Butterworth, or Chebishev design. The circuits employed can be:

1. Series
2. Shunt
3. Full series
4. Full shunt
5. "T"
6. Bridged "T"
7. Lattice type

Both of these circuits are characterized by input and output impedances that change with frequency.

These circuits maintain a constant input impedance but the output impedance varies with frequency.

These three circuits are identified by constant input and output impedances.

Equalizers and filters can further be of the balanced or unbalanced circuit configuration. Because of the 2-to-1 cost consideration and the very short length transmission paths inside a professional audio console, most equalizers and filters are of the unbalanced type. Any transmission circuits that enter or leave the console, however, are balanced and isolated from the unbalanced console circuitry by the use of high-quality repeat coils (isolation transformers).

Circuits Used Commercially

The devices discussed in this article are all of the four-terminal constant-K, unbalanced-circuit, passive, bridged-T type. The preferred impedance is 600 ohms, though 150 ohms as well as other values are encountered in the use of such devices.

Advantages of Passive Controls

The advantages of using such a passive control can be summarized as follows:

1. Very low design cost compared to a really stable active circuit.
2. Less complicated to build and to use.

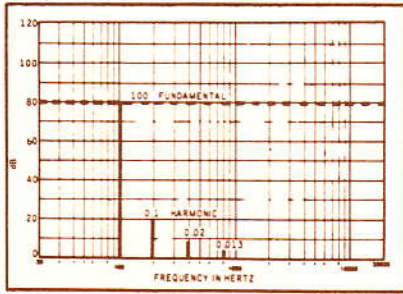


Fig. 1. True distortion of a circuit with the frequency response of Fig. 2.

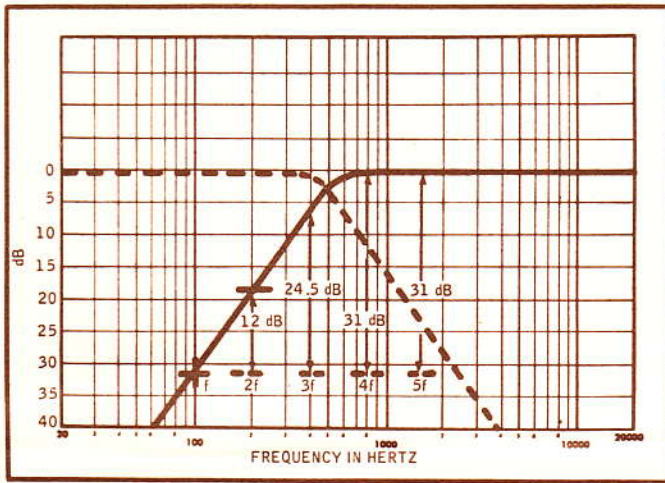


Fig. 2. Effect of frequency response on measured distortion figures.

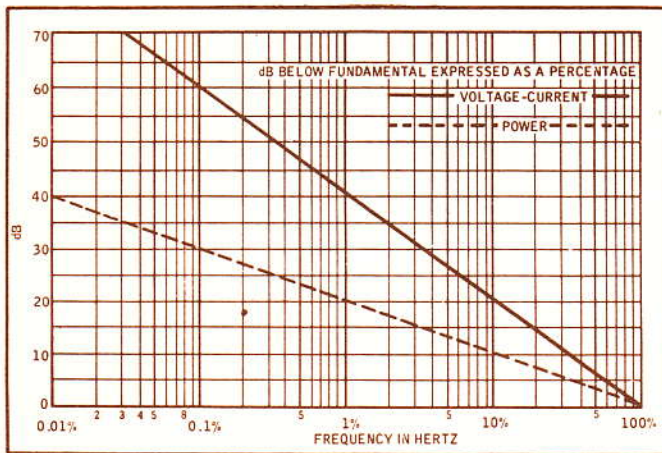


Fig. 3. Chart showing percentage derived from measurement of distortion as the number of dB below the fundamental.

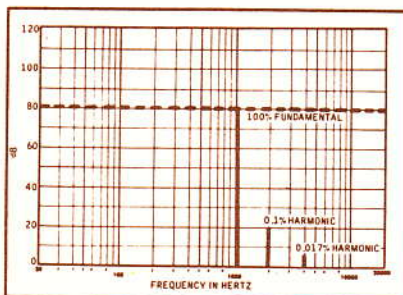


Fig. 4. Distribution of harmonics in a flat-response system.

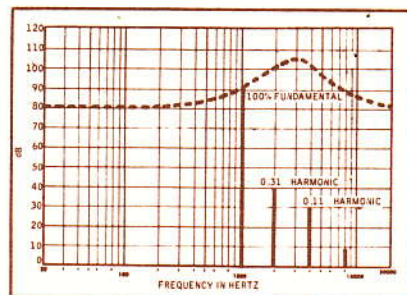


Fig. 5. Distribution of harmonics in a system with a "boosted" response.

3. More reliable over long time intervals. Greater repeatable accuracy.

4. More versatile. It can be used in system after system because it is an independent component.

5. Extremely low maintenance costs.

6. Minimum distortion that remains constant. No circuit changes in amplifiers will change the inherently low distortion figure of the controls. (Not measurable.)

Precautions to Observe

It is possible in the design of active circuits to "magnify" the "Q" of an inductance used, thereby allowing smaller sized components to be employed. When passive devices are used, particularly at low frequencies, size and weight of the components required will not lend themselves to miniaturization. Due to the high "Q" coils employed in passive equalizers care should be exercised when they are employed near appreciably high flux fields.

Distortion Measurements Pose Special Problem

Finally, it should be recognized that any frequency-response curve with a changing amplitude characteristic makes distortion measurements difficult. A typical example is the measurement of distortion in a crossover-network where the technician begins at a frequency that is on the slope of the network's response. Let's say that the real distortion characteristic looks like the chart shown in Fig. 1. Figure 2 discloses the slope of a 12-dB-per-octave crossover network. If 100 Hz is chosen as the measuring frequency, then it can be seen that the second harmonic will be increased 12 dB due to the slope. From Fig. 3 it is obvious that a harmonic 60 dB below the fundamental represents 0.1 per cent distortion, but, due to the slope of the network, the 2nd harmonic is now 60 dB minus 12 dB below the fundamental or 48 dB below the fundamental which equals 0.4 per cent distortion. The 3rd harmonic was 74 dB below the fundamental or 0.02 per cent distortion. Now, because of the slope of the network's frequency response it is now 74 dB minus 24.5 dB below the fundamental, or 49.5 dB below the fundamental, and this equals a distortion indication of 0.32 per cent.

Measuring Distortion in Equalized Circuits

This same discrepancy can occur in the use of high frequency equalization. Figure 4 illustrates the distortion characteristics of a system at a "flat" setting, while Fig. 5 shows the apparent increase in distortion caused

by a high frequency boost of 12 dB at 3000 Hz. (Notice that the 100 per cent indication for the fundamental is also raised by the equalization process.) So far as the ear is concerned such boost sounds like a real increase in distortion and this effect puts a practical limit on high-frequency boost of about 12 dB.

Low-frequency boost can have the inverse effect by dropping the higher harmonics still lower in relation to the fundamental. (This may well be the reason low-quality package hi fi's are usually adjusted "bass" heavy by their users.)

Calculation of Correction Factor

To obtain an accurate harmonic distortion figure from a system with a rising high-frequency amplitude characteristic, take the measured distortion expressed in dB below the fundamental and add the dB increase due to the slope of the system. This total, converted to percentage, will equal the true distortion of the system. (dB measured distortion + dB slope increase = dB below fundamental.)

Other Considerations

Attention must be paid to the insertion loss of the device (equalizer) and the maximum and minimum levels required for satisfactory operation. In passive equalizers there are two choices that can be made regarding insertion loss. Because it is a passive device the only way to obtain "boost" is to attenuate all but the desired "boost" frequency. When this is done the "boost" frequency is higher, relatively, than the non-"boosted" frequencies. However, if we merely depressed the frequencies to be attenuated in order to "boost" the selected frequency, we would have a loss in level at all frequencies attenuated that would vary with each equalizer setting.

One way to achieve constant gain in the equalizer is to use an inverse loss attenuator in conjunction with the equalizer. The attenuator inserts loss at the "flat" setting and gradually removes it to the same degree that the majority of the bandpass is depressed to obtain equalization.

Preferred Method

In the equalizers to be discussed in this article a full bandpass insertion loss is chosen, usually 14 to 16 dB, and equalization restores the required amount of this loss to obtain selective boost at chosen frequencies. By this means the only level change encountered in the program material is that occasioned by "boosting" a selected frequency. The resulting increased level at that frequency is the sought-

after effect. The unequalized portion of the bandpass remains at a constant level.

Dynamic Range Determined

Passive equalizers and filters of the unbalanced, bridged-T, constant-K type illustrated in this article should be operated between the levels of -70 and +20 dBm. Figure 6 reveals the dynamic range, noise, and gain characteristics of a high-quality, fixed-gain, plug-in-type professional audio system amplifier. This same amplifier shown in Fig. 7 can be used as a preamplifier, booster, program, and even line amplifier by merely changing the "strapping" at its external socket connection. This allows a single type plug-in unit to be used interchangeably anywhere in the system and this minimizes the number of units required for maintenance back-up. Fixed-gain amplifiers of this type can be designed for optimum negative feedback and stability. Figure 6 shows that the maximum output for the unit (at less than 1 per cent THD 20 to 20,000 Hz) is +27 dBm. Since it has a fixed voltage gain of 45 dB terminated and 51 dB unterminated, the

maximum allowable input signal must not exceed -18 dB and -24 dB respectively.

With these figures in mind it can be seen that the maximum input signal into an equalizer placed just ahead of such an amplifier must not exceed -16 dB. (-16 dB)-(14 dB insertion loss) + (12 dB max. equalization) = -18 dB output at some selected frequency. If for one of a number of reasons the output from the equalizer exceeds this figure the use of a fixed loss pad can correct the level.

Fixed Parameters

Again referring to Fig. 6 the fixed parameters are seen to be maximum output level, maximum input signal level and the equivalent-input-noise figure (E.I.N.), and consequently, the maximum signal-to-noise ratio. The dynamic range and the minimum signal-to-noise ratio are parameters that are played against each other depending on the requirements at hand. In general the minimum signal-to-noise ratio need not exceed 10 dB with 25 to 30 exceptionally quiet. The maximum dynamic range available in a

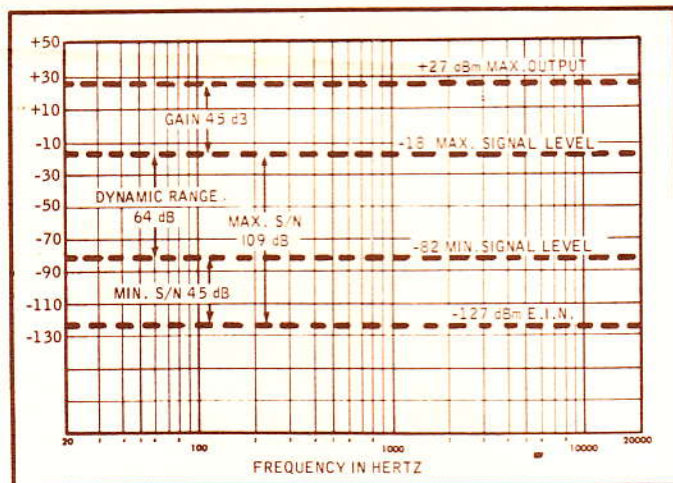


Fig. 6. Relation of dynamic range, noise, and gain characteristics of a high-quality fixed-gain professional amplifier.

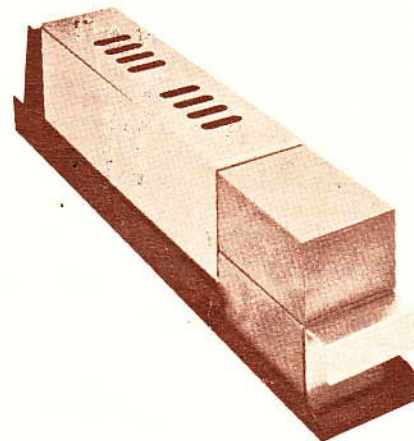


Fig. 7. Altec 9470A Amplifier, the type giving the characteristics of Fig. 6.

very quiet studio is shown in Fig. 8. The noise level shown is Noise Criterion Curve NC-20, and the maximum level shown in the maximum sound pressure level (SPL) in dB at

4 feet that can be expected from the best monitor speaker available. Since the figure shown, 93 dB, is the maximum dynamic range, it is also the maximum signal-to-noise ratio. Be-

cause the ear can barely hear sound below NC-20 any sound system with a maximum signal-to-noise ratio of better than 90 dB is going to have a noise level below that found in even the quietest acoustical environments.

The component that usually determines the noise threshold of the electronic part of the system is the power amplifier. Figure 9 gives the gain, maximum signal level, and maximum signal-to-noise ratios for the 20-watt professional monitor amplifier shown in Fig. 10.

Practical Limits to Dynamic Range

Figure 11 shows the dynamic range, and maximum and minimum signal-to-noise ratios required by a major recording company for their recording consoles, master tape recorders, master disc lathe, and finally, their production pressings. In the final analysis, the real determination of realistic dynamic range requirements and signal-to-noise specifications is the limits set by the source material. Even the finest professional tape recorder has a maximum signal-to-noise ratio that is 10 dB less than that achieved in the 20-watt amplifier shown in Fig. 10.

Another limitation of dynamic range in a listening system is the occasional use of a small "bookshelf" type speaker system with a mass loaded cone to help lower cone resonance in a too-small enclosure. Such loudspeakers exhibit a minimum level below which the inertia of the cone and the resistance of the suspension are not overcome by the signal. Once the input signal reaches a level of sufficient magnitude to overcome the friction and inertia, the loudspeaker suddenly "comes on." The transition from low-level output to no output is not continuous but is characterized by the loudspeaker "shutting off" below a critical level. The solution, of course, is replacement by a more efficient type of loudspeaker utilizing a lighter moving system.

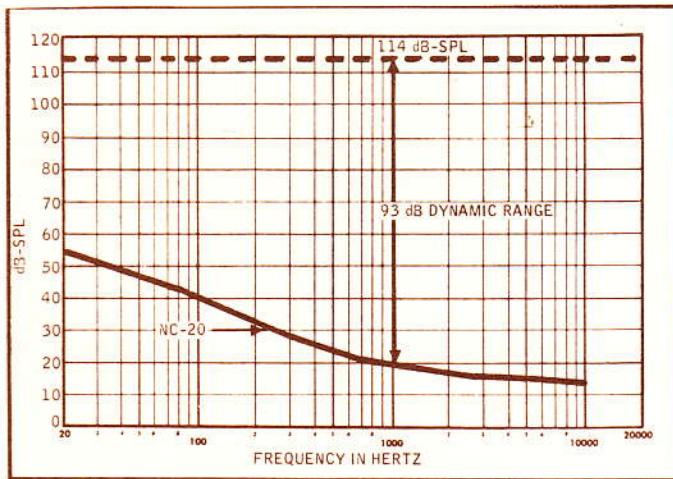


Fig. 8. Maximum dynamic range available in a quiet studio. The noise level shown in the Noise Criterion Curve NC-20.

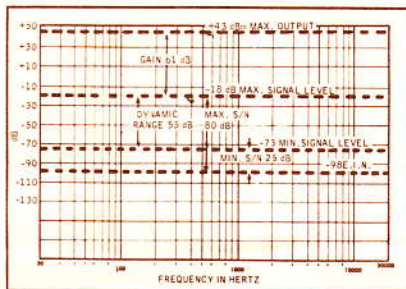


Fig. 9. Characteristics of a typical 20-watt professional-type monitor amplifier Altec 9471A, shown in Fig. 10.

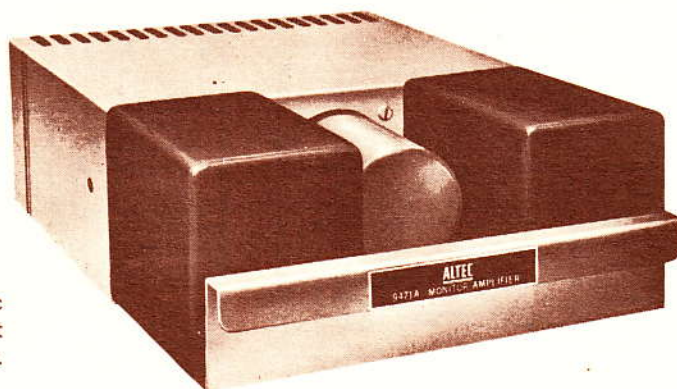


Fig. 10. The Altec 9471A, 20-watt monitor amplifier.

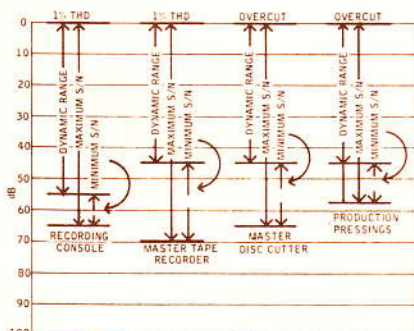


Fig. 11. Characteristics specified by a major recording company for various elements of their recording channels.

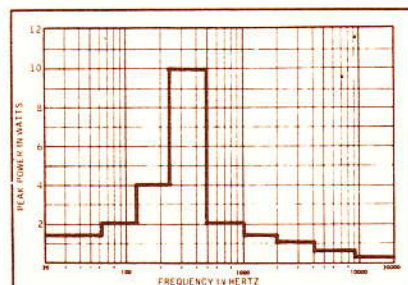


Fig. 12. Peak power per octave in a typical orchestral composition.

Energy Distribution of "Live" Source

One final consideration of dynamic range and equalization is that of the distribution of energy in typical source material. Figure 12 exhibits the peak power expressed in watts vs. frequency of a typical orchestral composition. It can easily be seen that consideration of equalization in the region of 125 Hz to 500 Hz requires careful consideration of maximum allowable input signal to the amplifier that follows such equalization. (For best results each program source should be individually studied to determine frequency distribution of energy.) AE

ALTEC LANSING



ALTEC's new Model 9704A transmission measuring set, precisely designed to accurately measure gain, loss, frequency response and signal levels of individual audio devices or complete installations.

Typical Equalizer and Filter Circuits

THE BASIC EQUALIZERS AND FILTERS, and the constant-K, unbalanced, bridged-T circuit for them, along with a sample response curve, are shown in Figs. 13 through 22.

A high-frequency rolloff is shown in Fig. 13, and a low-frequency rolloff is shown in Fig. 14. These are the types of circuit that is used in program-equalizer attenuation settings.

Figures 15 and 16 illustrate the circuits used to produce special effects or to eliminate interference that has a definite spectral frequency. The broadness or sharpness of these curves can be varied by a change in the L-C ratios.

Figures 17 and 18 give the circuits that are used to restore deliberate insertion losses to "shelved" type accentuation.

Figures 19 and 20 show frequency-selective attenuation and "boost" circuits. It is this type of circuit that is used in a typical high-frequency-boost-or-cut portion of a program equalizer or graphic equalizer.

Figures 21 and 22 consist of an 18-dB-per-octave low-pass and high-pass filter. These are extremely useful circuits for limiting the passband of a wide-range system to those frequencies which the transducers involved are capable of handling cleanly, thereby avoiding overload from frequencies not containing useful energy. Variable equalizers and filters are merely series of these basic circuits sequentially se-

lected by means of precision switches such as shown in Fig. 23.

Equalizers and filters of this type require careful termination in their rated impedance. Figure 24 diagrams the test set-up used to record the frequency response curves that follow.

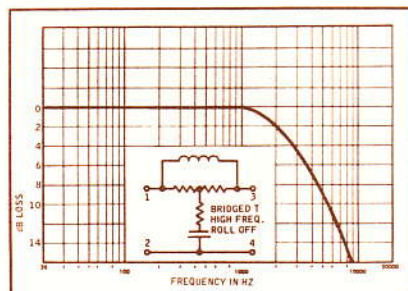


Fig. 13. Bridged-T high-frequency roll-off equalizer and its response curve.

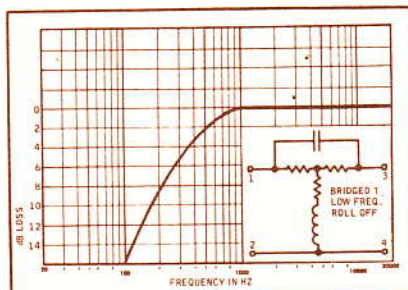


Fig. 14. Bridged-T low-frequency roll-off equalizer and its response curve.

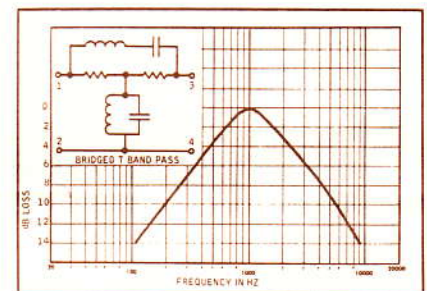


Fig. 15. Bridged-T band-pass equalizer and response curve.

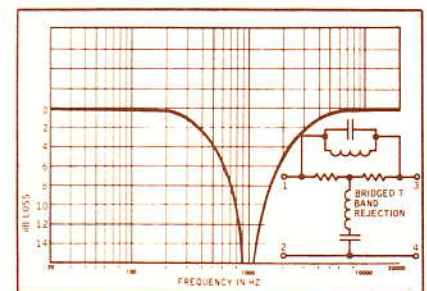


Fig. 16. Bridged-T band-rejection filter and response curve.

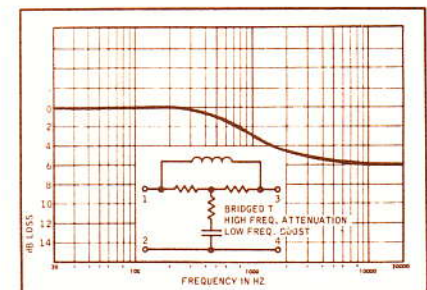


Fig. 17. Bridged-T "shelving" equalizer used to attenuate highs, boost lows, and the resulting response curve.

Design Laboratory Illustrated

The use of a servo-operated recorder-generator assembly allows automatic recording of the amplitude-frequency characteristics of equalizers and filters. Due to the reduced time such testing requires as compared to conventional hand plotting (and the reasonable cost of such test instruments today), high-quality professional equalizers and filters now come with such curves recorded for each individual unit. Figure 25 shows a laboratory where equalizers and filters are designed and measured. The output of the recorder-driven test oscillator shown at the lower right corner is flat within ± 0.5 dB over its entire frequency range.

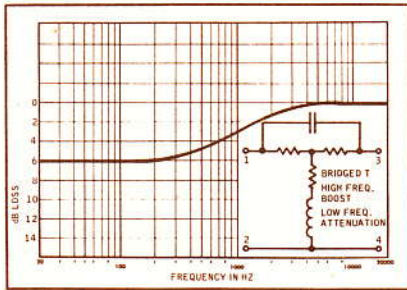


Fig. 18. Bridged-T "shelving" equalizer used to boost highs, attenuate lows, and its response curve.

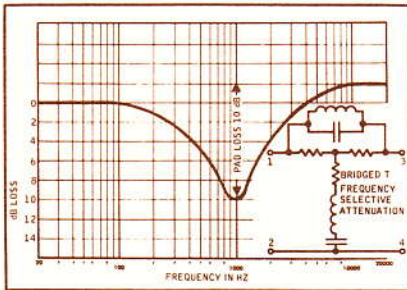


Fig. 19. Bridged-T frequency-selective equalizer used to eliminate or reduce unwanted peaks in response or to produce a desired effect.

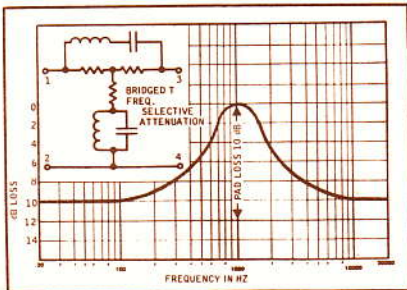


Fig. 20. Bridged-T frequency-selective equalizer used to increase output at a specific frequency.

Commercially Available

Passive Controls

Commercially available versions of passive equalizers and filters are available from a number of manufacturers. They take the form of microphone equalizers, program equalizers, graphic equalizers, filter sets, and fixed pre- and post-equalizers.

Microphone or Dialogue Equalizer

A microphone equalizer and its plug-in mounting bracket are shown in Fig. 26. This is a series of passive LCR bridged-T, constant-K networks with input and output impedances of 600 ohms. The insertion loss at the "0" or flat setting of the controls is 14 dB. It provides low-frequency shelving at 100 Hz and high-frequency boost at 7 kHz. Maximum boost available at each of these frequencies is 12 dB. It also provides selective attenuation in 2-dB steps up to a maximum of 16 dB at 10 kHz and 16 dB at 100 Hz, as shown in the curve of Fig. 27.

This figure shows the frequency-response curve of it at its flat setting, and then one run at maximum bass boost/maximum treble roll off, and another at maximum bass roll off/maximum treble boost.

Program Equalizers

Figure 28 shows a more sophisticated version of the microphone equalizer which is known as a program equalizer. The internal construction showing the mechanical means

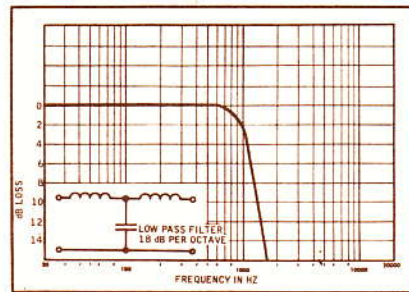


Fig. 21. 18-dB/octave low-pass filter and its response curve.

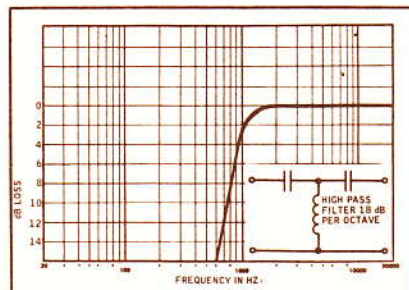


Fig. 22. 18-dB/octave high-pass filter.

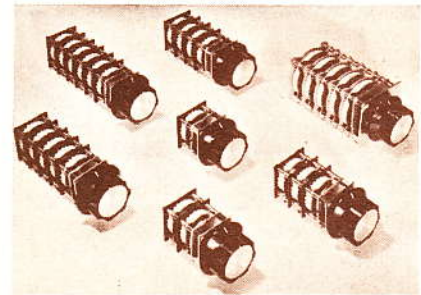


Fig. 23. Precision switches used for attenuators and equalizers in professional audio systems.

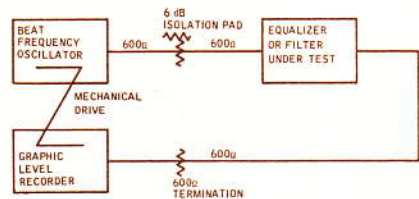


Fig. 24. Block diagram of measurement method employed to record response curves automatically.

of selecting the large number of network-circuit combinations represented illustrates why most of those in use are commercially manufactured units. Equalizers like the microphone unit previously shown are used principally as dialogue equalizers or to correct room problems in a sound stage or studio. Program equalizers, on the other hand, are designed with the playback system in mind as well as the recording system. In addition to its attenuation and boost functions, in 2-dB increments, it allows a choice of two low-frequency shelves at 100 and 40 Hz at the calibrated points and four high-frequency-boost points—3, 5, 10, and 15 kHz. The functions desired are selected by the two knobs at the top of the panel.

On the low-frequency shelving switch are two "off" positions that bypass the entire equalizer and insert a 14-dB loss pad in its place. This allows instant aural comparison between equalized response and "flat" response at the turn of a switch.

Amplitude Response Curves

Figure 29 displays a composite frequency-response chart of the low-frequency shelving at 40 Hz and high-frequency boost at 10 kHz for different amounts of attenuation at each of the steps available. Note that the shelving control affects only the boost portion of the equalizer's response. Similar curves would result from the

Professional Audio Controls

100-Hz setting, but would simply be moved up the frequency scale about $1\frac{1}{2}$ octaves. The high-frequency boost selector was set at 10 kHz although 3-, 5-, and 15 kHz positions are also available. Note here also that the high-frequency boost selector affects only the boost functions of the equalizer. These units are usable in any 600-ohm circuit by simply inserting them in the transmission line at the proper level. A wide variety of response curves can be obtained with this type of equalizer.

Graphic Equalizers

A graphic equalizer is shown in Fig. 30. This equalizer allows exceptional control of a signal from 50 to 12,500 Hz. The unit shown consists of 7 boost and 7 attenuate equalizers covering a range from +8 and -8 dB. The total unit has an insertion loss of 16 dB with all controls set at "0" or "flat" position. Each control operates in 1-dB increments. Again, the circuits employed are bridged-T, constant-K, passive networks, designed for use in 600-ohm lines. The special effects possible with this unit range from an "other worldly" voice of the ghost in Hamlet to increased "presence" on a distant microphone pick-up. The operator's imagination is about the only limitation the instrument imposes. The curves of Fig. 31 were recorded by measuring each boost setting and each attenuate setting individually at its top and bottom position. This enables one to see the individual filter shapes associated with each control. Where the filter "skirts" cross, interaction occurs if two adjacent controls are used simultaneously. This allows smooth continuous curves to be formed.

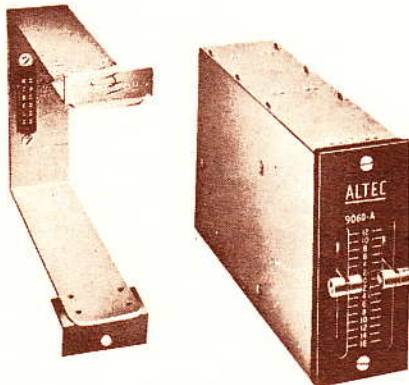


Fig. 26. Altec 9060-A microphone equalizer and its mounting fixture.

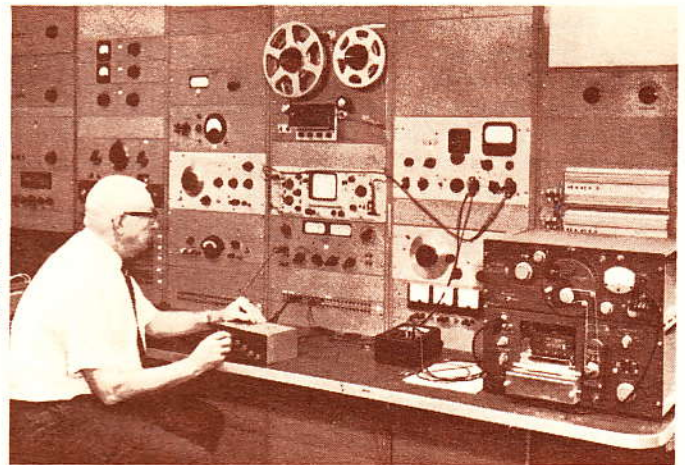


Fig. 25. Co-author Arthur Davis measures response of a graphic equalizer. Note automatic curve-tracing equipment at lower right corner.

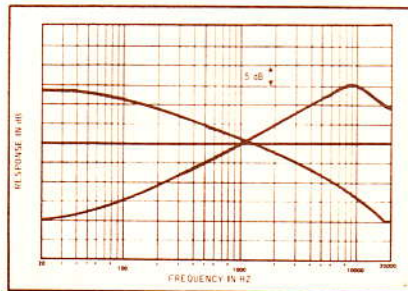


Fig. 27. Limits of curves obtainable with the microphone equalizer of Fig. 26.

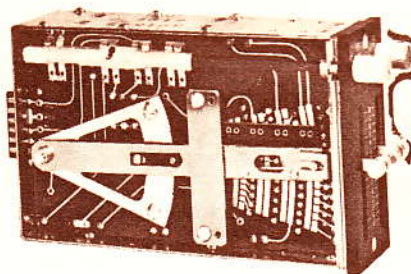


Fig. 28. Program equalizer which will provide the wide variety of curves shown in Fig. 29. Any combination of these curves may be obtained.

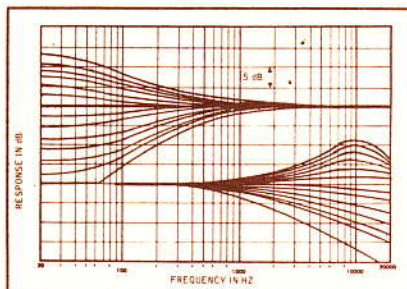


Fig. 29. Composite of curves obtainable with equalizer of Fig. 28.

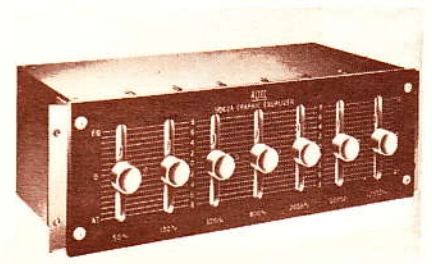


Fig. 30. Graphic Equalizer which will permit boost or cut of 8 dB at any of seven frequencies approximately $1\frac{1}{2}$ octaves apart. One, two, three, or all of the controls may be varied to achieve the desired effect.


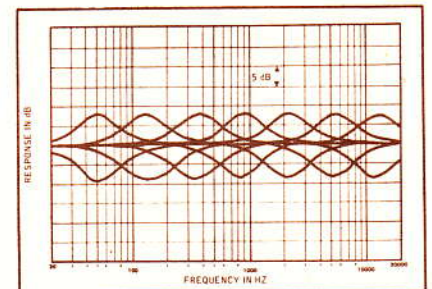


Fig. 31. Composite of 14 individual curves, each of which was run with a single control at its extremes. Superimposed, they appear as shown. If all controls were put at +8, for example, the resultant curve would be practically flat at the +8 level, and similarly would be practically flat at the -8 level if all controls were placed at -8.

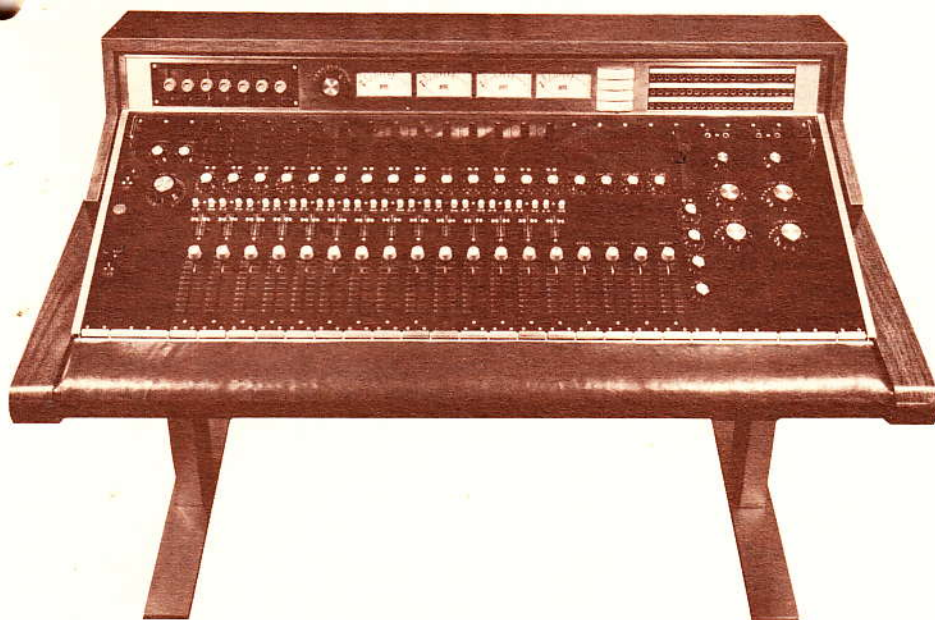

ALTEC's sensational new Model 9200 professional console — a basic modular type enclosure for assembly by the user from Altec catalog components to meet his individual requirements. User purchases the basic cabinet and hardware, drilled, punched and beautifully finished — all difficult metal work is done. He then selects desired Altec modules to complete the console in accordance with his needs.



Fig. 32. Typical filter set providing eight cutoff frequencies for the high-pass section, and eight for the low-pass section. It is capable of producing response curves like those shown in Fig. 33.

Use of Filters

Once equalization is accomplished, consideration should then be given to the filters desired to maintain the integrity of the passband of interest to the user. A tremendous source of distortion and overload in audio systems lies in building the system to *try* to reproduce frequencies of no use to the program material actually desired. (This is not to be confused with the concept of designing very-wide-range components in the effort to minimize phase shift in the passband of interest.)

In a quality system it is foolish to feed a well designed loudspeaker high-amplitude signals below its lowest rated frequency. When there is doubt about source material (turntable rumble cut into the record, eccentric record due to misplaced center hole, and so on) a high- and low-pass filter set, in this case, at the input, saves the system from amplifying, controlling, and attempting to reproduce gross defects.

Figure 32 shows such a filter set with multiple choices of cut-off frequencies. Such filters can also be constructed as fixed type units, but are obviously not as flexible in use.

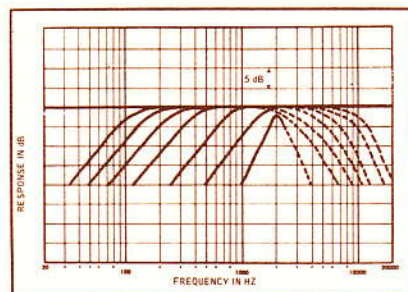


Fig. 33. Reponse curves available from the filter shown in Fig. 32. A wide variety of effects can be created with this type of filter.

Figure 33 shows the various cutoffs obtainable with different control settings. The high-pass curves are shown solid, the low-pass ones dashed. The overlap of the cut-off frequencies at each end of the spectrum allow the unit to be used as a simple form of bandpass analyzer. Here, once again, the circuit is a series of bridged-T, constant-K, passive 600-ohm networks wired to precision rotary switches in order to permit variable choices.

Filters are characterized by no insertion loss until their cut-off, F_c by definition is the point where the amplitude response has fallen 3-dB and these filters follow that convention.

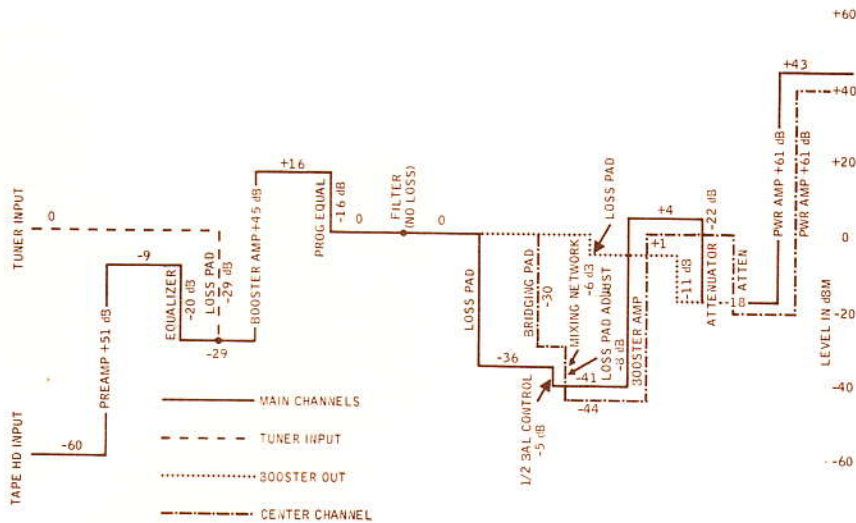


Fig. 35. Level diagram of the circuit of Fig. 34. This type of diagram gives an immediate picture of the various levels throughout the system—of greatest importance in the design.

At this point another adjustable loss pad is encountered which enables the center channel to be adjusted 3 dB lower than the two side channels. (Acoustical mixing of the two side-channel speakers provides a substantial acoustical middle-channel signal. If the physical middle-channel speaker is set to a level equal to the two side channels, its output plus the side channels gives an apparent output from the center that is too high.) The presence of adjustable loss pads in each channel allows for any gain balance desired or required under difficult room environments, or to allow different-channel gain balances to suit individual ears. Once the system is properly adjusted for a given space and use, the variable controls provide more than sufficient day-to-day and source-to-source adjustment.

Wiring & Grounding the System

Although this subject could easily fill a large book, a few suggestions may be helpful.

All wiring in audio systems of this type should be done with two-conductor shielded cable (usually with a solid shield wire in addition to the shield), and with the shield insulated. The low side of every network is carried through on one of the two conductors to the single system ground. All grounds are connected at the same spot. Shields are grounded at one end only and each run between components should be made with only one end of the shield being grounded. The other end of the shield is left disconnected. Even with these precautions, the wiring in such systems is relatively straightforward.

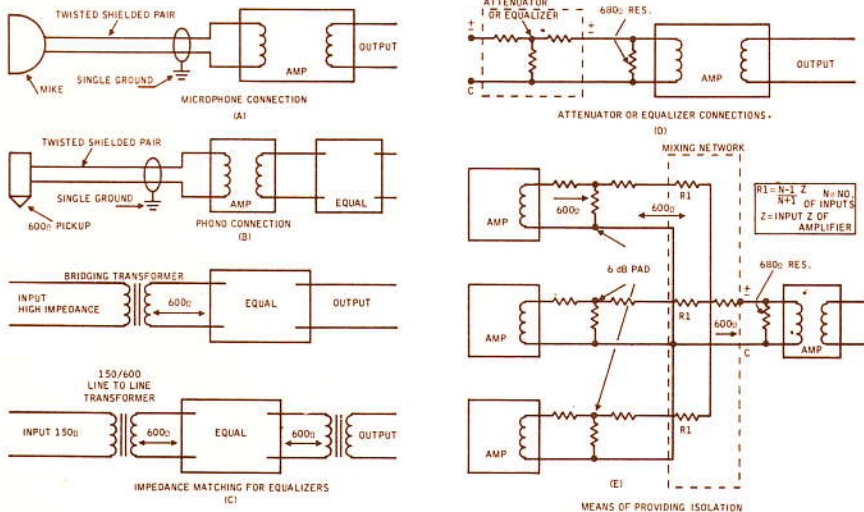


Fig. 36. Several acceptable ways of connecting passive equalizers into a system, and methods of providing isolation between circuit elements which might interact to cause response irregularities.

Summary


It is obvious that the professional audio engineer has a much wider choice of components than the home user. The components are also of higher quality and usually of far greater accuracy and re-setability. Best of all, as the years pass the old equipment isn't discarded. The basic quality components can be expanded or rearranged to meet new requirements.

It is hoped that the dedicated sound-system designer will consider stepping up from high fidelity components to the use of professional passive-control/fixed-gain playback systems with their advantages of better performance, longer life, and lower cost. AE

Bibliography for further study.

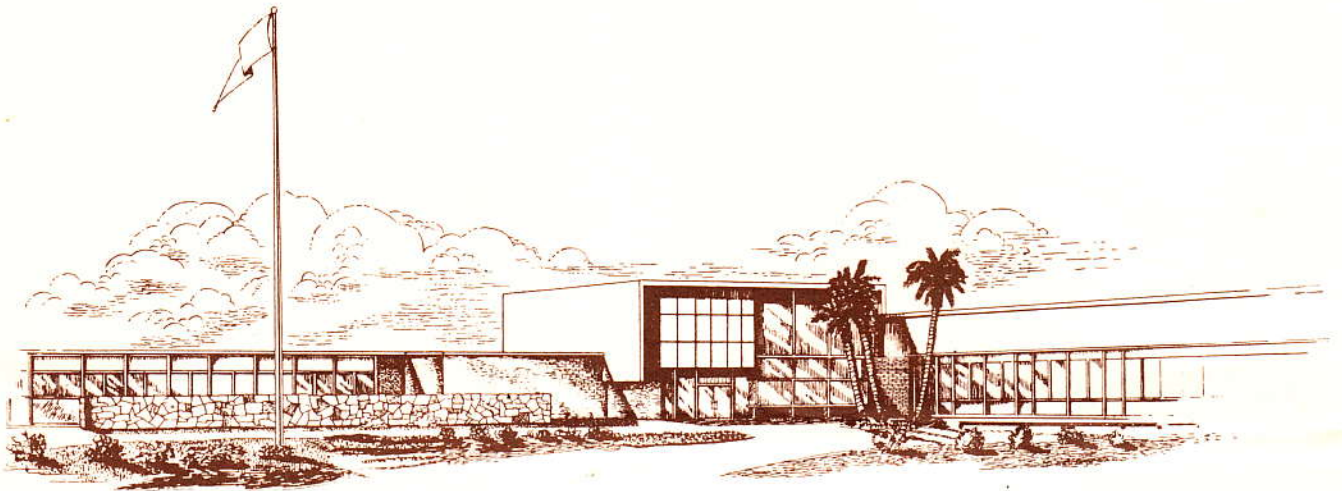1. "Motion Picture Sound Engineering." Research Council of the Academy of Motion Picture Arts and Sciences: D. Van Nostrand Co., Inc. 1938.
2. Frederick Emmons Terman, "Radio Engineer's Handbook." New York: McGraw-Hill Book Co., Inc. 1943. (Particularly the chapter on Circuit Theory, where the phase-area theorem is discussed.)
3. "Reference Data for Radio Engineers." 4th Edition. International Telephone and Telegraph Corp.
4. Robert W. Landee, "Electronic Designer's Handbook." New York: McGraw-Hill Book Co., Inc. 1957.
5. Howard M. Tremaine, "The Audio Cyclopedica." Indianapolis: Howard W. Sams, Co., Inc. 1959.
6. Howard M. Tremaine, and George K. Tefreau, "Attenuators, Equalizers, and Filters." Indianapolis, Ind.: Howard W. Sams, Co., Inc. 1956.
7. Howard M. Tremaine, "Passive Audio Network Design." Indianapolis: Howard W. Sams Co., Inc. 1964.
8. Julian L. Bernstein, "Audio Systems." New York: John Wiley & Sons, Inc.
9. Hendrik W. Bode, "Network Analysis and Feedback Amplifier Design." Princeton, J. J.: D. Van Nostrand Co., Inc. 1945. (Chapter XI portion on Minimum-Phase-Shift Networks, and Chapter XII, Topics in the Design of Equalizers.)
10. James Moir, "High Quality Sound Reproduction." New York: The Macmillan Co., 1958. (Contains data from paper on "Auditory Perspective" Symposium by Bell Lab. Engrs. *Electrical Engineering*, Jan. 1934.
11. Oliver Read, "The Recording and Reproduction of Sound." Indianapolis: Howard W. Sams & Co., Inc.
12. John G. Frayne and Halley Wolfe, "Sound Recording", New York: John Wiley and Sons, Inc. 1949.

Reference to these works and the further bibliographies they contain will provide a good conceptual view of design requirements pertinent to passive attenuators, equalizers and filters.



1515 SOUTH MANCHESTER AVE. ANAHEIM, CALIFORNIA • 92803



A Division of *LSV* Ling Altec, Inc.

AL 1365