
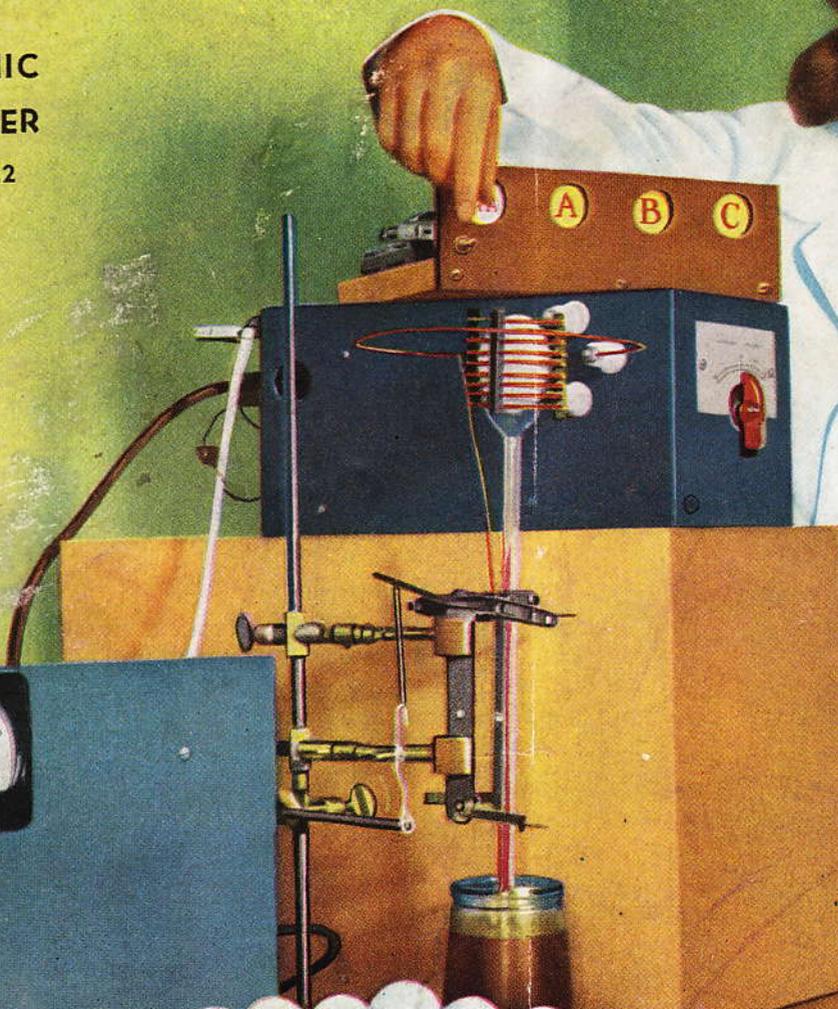


# RADIO CRAFT

K

ELECTRONIC  
EGG GRADER  
SEE PAGE 22

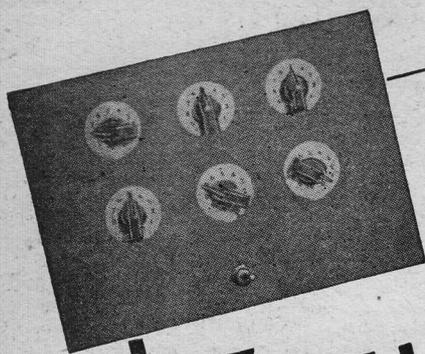



# Response Equalization

By J. W. STRAEDE

**M**OST reproducing or recording systems require some form of frequency response correction. The bass or lower frequencies may be attenuated in recording or high frequencies may need emphasizing after passing through a selective radio tuner.

The majority of "tone controls" affect the high-frequency response only, and then only between fixed limits. A few amplifiers are provided with attenuators for low frequencies, but again the rate of attenuation and frequency from which attenuation starts are fixed.

In the system described here, the bass attenuation may start at any of 5 (or more) frequencies, the attenuation may be kept constant below a given frequency or the amount of attenuation may be varied. But that is not all. The lower frequencies may be emphasized or boosted below any of 5 (or more) frequencies, and the amount of boost is controllable. *It is even possible to boost some low frequencies while attenuating others.*

The same thing goes for the high-frequency end of the spectrum, except that in the practical version of the circuit, no provision is made for rate of attenuation above a determined frequency and, instead, sharper cutoff is provided as this is generally more useful.

## Response correction types

What are the commonly required types of response correction? There are bass attenuation combined with slight high-frequency boost for ordinary recording, bass boost with extreme high-

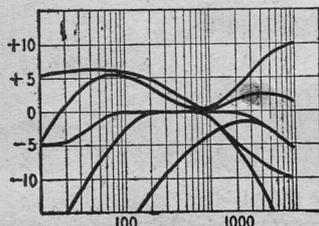


Fig. 1—A few forms of response correction.

frequency boost for orthacoustic recording, the opposites of these first two for reproduction; large bass boost at very low frequencies below the main speaker resonances, high-frequency equalization for good crystal pickups, and the same with a boost of only the infra-low bass for cheaper crystal pickups.

Some of the possible frequency corrections are shown in Fig. 1, a maximum variation of about 10 db being obtainable except for the high-frequency attenuation which can be obtained at the rate of about 12 db per octave.

## Simple circuit used

These boosts and attenuations are obtained with a relatively simple circuit. There are no multigang potentiometers, no inductance to pick up hum, and no nonstandard parts. All the work is done by ordinary radio resistors, condensers,

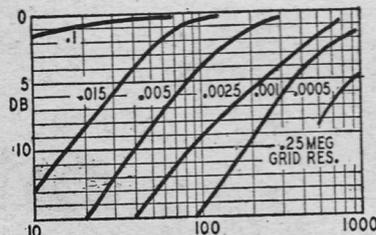


Fig. 2—Effect of coupling condenser on lows.

switches, and potentiometers. The tolerance of the resistors may be 10% and that of the condensers 15% before any noticeable effect occurs (unless, of course, the circuit is used to equalize some amplifier within 1 db for laboratory work).

The whole job is very compact if the power supply is taken from the rest of the amplifier. The single 6J7 or 6SJ7 tube provides a mid-frequency gain of about 10 db after loss in the circuit has been allowed for. All the results are obtained by well-known circuit networks.

## Coupling condensers

It is well known that coupling condenser size affects low-frequency re-

sponse. What is not so well known is that the size of the condenser also determines the frequency from which bass attenuation takes place (that frequency is the one at which attenuation is 2 db). The rate of attenuation is approximately 6db per octave and this rate does *not* depend on condenser size.

In most recording work, the attenuation must start from 250 to 700 cycles, while in public address work the bass cut must begin at about 1,000 cycles when maximum intelligibility and extreme audibility are required. So the first step in designing the circuit was to provide a variable coupling condenser (actually a number of condensers controlled by a simple 5-way switch). A simple rule for determining the frequency at which attenuation commences is

$$f = \frac{R}{5C}$$

where R is the grid resistance in megohms and C is the size of coupling condenser in microfarads. The effects of these condensers is shown in Fig. 2. It might be argued that only a limited number of capacitances is obtainable, but in practice the capacitance is not at all critical.

Amount of low-frequency attenuation is controlled by varying a resistance shunted across the coupling condenser (see Fig. 3). Actually the maximum value of the variable resistance limits the amount of attenuation obtainable—this is usually not of importance, but if necessary the end of the resistance element can be scraped away so that circuit can be opened completely.

## Low-frequency boost

The method for boosting the bass is to attenuate to a fixed degree all frequencies above a certain point. This is done by a voltage divider such as is shown in Fig. 4, the lower arm consisting of a resistor and condenser in series. The frequency below which the boost starts is controlled by the condenser size, the maximum rate of boost being

nearly 6 db per octave. Just where the bass boost is to be introduced is decided by the work to be done. When English records are to be played with a "flat" pickup, the boost should commence at about 250 cycles, while for American


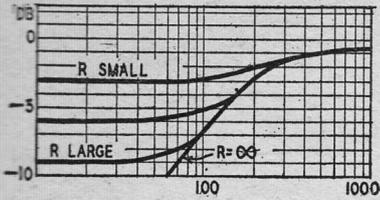


Fig. 3—Bass attenuation control and its effect on tone.

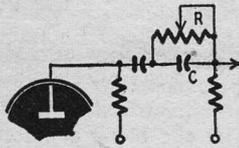

records the boost should start nearer the 700 cycle mark.

To reduce the amount of bass boost the condenser is shunted by a variable resistor. It should be noted that the graphs of Figs. 3 and 4 are similar except that one is inverted; but remember that the bass boost and bass cut can start at different frequencies so that a hump or a dip may be obtained around some frequency.

In Fig. 5 the complete circuit for low-frequency compensation is shown. The values are those which have been found most suitable in practice. Remember that resistor size controls amount of attenuation while condenser size controls the frequency at which a cut or boost commences.

### High-frequency equalization

It is well known that high-frequency signals can be attenuated by shunting a condenser between the plate and cathode of a tube. The rate of attenuation at higher frequencies is 6 db per octave, the starting frequency being decided by the type of tube, size of load resistor, and size of shunt condenser. (The load resistor includes the grid resistor effectively connected in parallel as regards h.f. with the resistor that goes to the high-frequency supply.)

For a given product of capacitance and load resistance, a pentode tube gives greater attenuation than a triode, an approximate formula for the attenuation of a pentode being:

$$\text{Attenuation in db} = 20 \log \frac{X_c}{\sqrt{R^2 + X_c^2}}$$

where R is resistance of the load and X<sub>c</sub> the reactance of the shunt capacitor

$$(X_c = \frac{1}{2\pi f C})$$

where f is the frequency in cycles per second and C is the capacitance in farads).

Such a shunt condenser may not provide sufficiently sharp cutoff. An extra attenuation of nearly the same rate may be obtained by using another shunt condenser at a later point in our circuit, for example, after the 1/4-megohm resistor that supplies signal to the bass-boost network. The reactance of

this condenser, as a first approximation, should bear the same ratio to the 0.025-megohm resistor as the anode shunt condenser bears to the 0.1-megohm anode resistor.

To prevent too much attenuation of the highs when ordinary records (which have only a limited h.f. boost) are played, a resistor may be connected in series with the by-pass condensers, although most people seem to prefer fairly sharp attenuation. High-frequency boosting is wanted for recording and for the realistic reproduction of speech—the former requires a boost commencing at about 1,000 cycles, the latter from 5,000 cycles or from wherever the microphone and speaker performance begin to fall off.

The easiest way to obtain the boost is to connect a small condenser in paral-

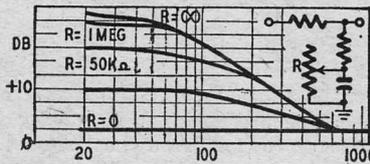


Fig. 4—Circuit and effect of bass booster.

lel with the 1/4-megohm resistor that reduces the mid-frequency gain by about 20 db. This shunt condenser reduces the

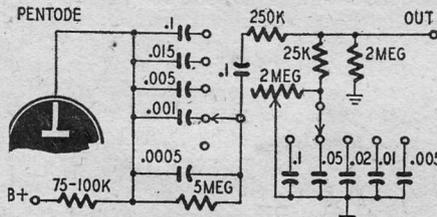


Fig. 5—Practical low-frequency compensator.

loss from over 20 db to about 11 db at high frequencies, so an effective boost of nearly 10 db is obtained. Just as in the rest of the circuit, the capacitance of the condenser is inversely proportional to the frequency at which any given amount of boost occurs, a small condenser of the order of 100 micro-microfarads being required for boosting the frequencies around 10 kilocycles, and about 10 times this capacitance for recording. As shown in Fig. 6, a switch is used to change the capaci-

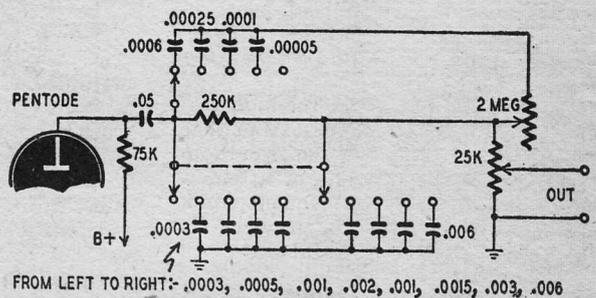


Fig. 6—Circuit for boost and attenuation of the high frequencies.

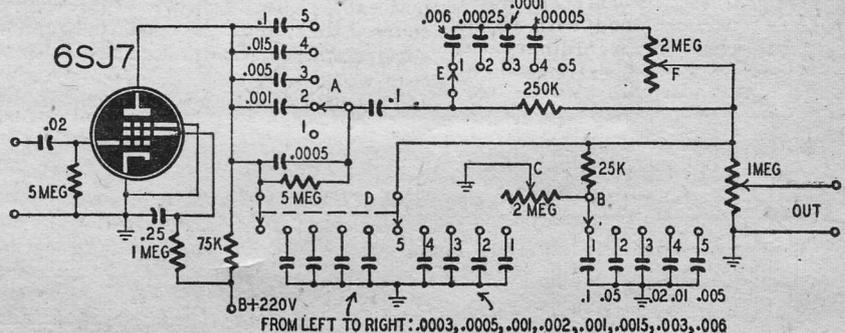


Fig. 7—This complete practical circuit combines all the features of previous figures.

tance. To control the amount of boost and to keep the rise in gain limited to a certain frequency band, a variable resistor is connected in series with the boost condenser.

Fig. 7 is the final practical circuit. A controls the frequency of bass cut, and B the frequency of bass boost. C controls the amount of bass boost. D varies the frequency of cutoff of highs, while E controls the frequency of high boost, and F its amount.

This final circuit is simplified by omitting the variable resistor that had been connected in series with the high-frequency attenuating condensers and also the variable resistor that had been connected across the low-frequency attenuating condensers. It was found that it was far more important to be able to control the frequencies at which attenuation started than to control the amount of attenuation.

### Setting of controls


For recording on discs, the low-frequency attenuator (A in Fig. 7) is set to give a fair amount of attenuation. If the recording is done at over 100 lines per inch, the 0.001-μf coupling condenser is used, otherwise the 0.005-μf condenser gives enough reduction. Pipe-organ and dance-band music usually require greater attenuation than a female chorus or soprano singer. If an orthacoustic response is required, a bass boost is provided at the very low frequencies by turning the 2-megohm resistor C to maximum value and setting B to 0.05 μf. Otherwise C is left at minimum resistance and the setting of B is unimportant.

The high-frequency attenuator D is turned off and the high-frequency boost controls are adjusted. E is set to about the middle position and F adjusted to a value of about 0.25 megohm (for a boost of about 5 db).

(Continued on page 77)



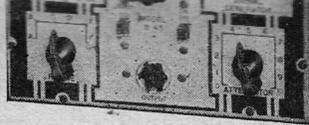... but rush your order anyhow. We guarantee to refund your money in full if the units do not meet with your complete approval after a 10-day FREE trial.



**Specifications of Model M-50**

- Accurate Pocket size 1000 ohms per volt V.O.M.
- 4 A.C. VOLTAGE RANGES: 0-15/75/300/1500 volts.
- 4 D.C. VOLTAGE RANGES: 0-15/75/300/1500 volts.
- 2 D.C. CURRENT RANGES: 0-15/150 MA.
- 2 RESISTANCE RANGES: 0-10,000 ohms; 0-1 Megohm.
- Attractive modern black & white panel.
- Beautiful hand-rubbed oak case. Complete with test leads and all operating instructions.

**Specifications of Model M-50**

Generates RF frequencies from 150 Kc. to 50 Mc. Modulation is accomplished by grid-blocking action—equally effective for alignment amplitude and frequency modulation as well as for television receiver. Self-contained batteries. All calibrations etched on front panel. DIRECT READING. Beautiful processed dualtone front panel heavy gauge crystalline steel cabinet. Complete with test leads self contained batteries.

20% deposit required on all C.O.D. orders.

**MOSS ELECTRONIC DISTRIBUTING CO.**

68 WESTCHESTER SQ.  
Dept. RC-9 New York 61,

**RESPONSE EQUALIZATION**

(Continued from page 35)

When playing back, the position is quite different. Unless orthacoustic recordings are to be played, there is no low-frequency attenuation. A is set to 0.1 µf (to 0.005 µf for orthacoustic), and a bass boost is provided by setting C to maximum value and then adjusting B for the frequency at which the boost is to begin, 0.01 to 0.02-µf being the values generally employed.

For public-address work with a good microphone, the controls are set as follows:

A to 0.005-µf; B, anywhere; C, at minimum resistance; D, off; E, at 50 µf; F, at minimum resistance or about 0.25 megohm.

The setting assumes that a good speaker is to be used and the amplifier is not being overrun. If as much intelligible sound as possible is required without regard to naturalness, then the setting is modified to:

A, at minimum capacity; B, anywhere; C, off; D, at from 0.0005/0.0015 µf (middle position); E, at from 0.00025 µf or 0.0006 µf; F, at almost minimum resistance.

The 6 controls (and an on-off switch) are mounted on a panel 10 inches by 7 inches, and a metal case affords screening against hum. A much smaller case could have been used, but space was allowed for a power-pack.

**NEW LOW PRICE**

**SPEAKERS**

- 5" P.M. Alnico 5 Magnet, \$1.09 each
- 6 for \$6.00
- 6" P.M. 2.15 oz. Alnico 5 Magnet, 1.69 each
- 6 for \$9.00

All other sizes in stock, at money-saving prices.

**AUTO RADIO SUPPLIES**

- OZ4 TUBES, each..... 89c
- Minimum order, 6
- SPARK Plug SUPPRESSORS.11
- See our Catalog for full line of auto aeriels.

**PHONO SUPPLIES**

- Crystal Pickup Arms..... 2.49
- Webster No. 50 Changer. 21.17
- Webster No. 56 Changer. 26.66
- Webster No. 70 Changer. 43.20
- Free \$2.50 permanent needle with each changer.

**Volume Controls**

- 1/2 MEG. volume control with switch and long shaft, ea. 49c
- 6 for \$2.75

**Money KITS Saving**

- 100 Insulated Resistors, 1/2, 1 & 2 Watt..... \$1.95
- 20 Assorted Wire Wound resistors... 1.95
- 50 Popular Assorted Mica Condensers.. 2.50
- 20 Assorted Tube Sockets..... 1.00
- 20 Assorted Trimmers 1.00
- 15 ASSORTED VOLUME AND TONE CONTROLS (less switches) ..... \$1.95
- I.F.'s 455 KC..... 39c

**WIRE**

- 400 ft. (approx.) of wire in assorted colors and gauges, solid & stranded in 2 to 4 feet lengths, per pkg..... 99c

**CONDENSERS**

Tubular	Paper (600 V)	Wfg.	Price Ea.	Per
.01	.08		\$ 6.	
.02	.08		6.	
.05	.10		8.	
.1	.12		9.	
.25	.17		13.	
.001	.08		6.	
.002	.08		6.	
.005	.08		6.	
.006	.08		6.	
.5	.26		22.	
<b>"Illinois" Electrolytic</b>				
mfd.	VDC		Price	
10	25v			
100	25v			
12	50v			
16	150v			
20	150v			
24	150v			
30	150v			
50	150v			
8	450v			
10	450v			
16	450v			
20	450v			
40	450v			
100	15v			
<b>"Illinois" Dual</b>				
16-16	150v			
20-20	150v			
30-30	150v			
40-20	150v			
50-30	150v			
8-8	450v			
10-10	450v			
20-20-20	150v			

10% discount on all electro purchased in lots of 10 or more. Mica Condensers, all sizes.

**HEAVY DUTY POWER TRANSFORMER**

Thordarson T70R62. 115V. 60 Cycle primary. Secondary 700 V.C.T. @ 145ma., 6.3V. winding @ 4.5 amps; 5V. winding @ 3 amps. Special price while limited quantity \$3.95 lasts.....

Minimum Order \$3.00—20% with order, Balance C.O.D.—WRITE FOR CATALOG. TWO CONVENIENT PLACES FROM WHICH TO ORDER. PLEASE ADDRESS DEPT. C9  
**ELECTRONIC DISTRIBUTORS, INC.**  
620 W. Randolph St., Chicago 6, Ill

**12lbs. SURPLUS ELEC-TRONIC PARTS \$2.00**

A gold mine of parts for repairmen, amateurs, and hobbyists. sockets, condensers, resistors, transistors, coils, hardware, wire, etc., etc. An outstanding in usable parts! Send \$2.00 cash, check or M.O. (Pay small express charges on receipt.)

**ELECTRONIC PARTS CO.**  
436 W. State St., Milwaukee 6