

# RADIO — ELECTRONICS

LATEST IN  
TELEVISION  
SERVICING  
AUDIO

formerly

**RADIO  
CRAFT**

HUGO GERNSBACK, Editor



SEPT

1950

30¢

U. S. and  
CANADA

↑  
FASTER PICTURE TUBE PRODUCTION — SEE TELEVISION SECTION

# A High-Gain Amplifier

**B**UILT for use in a dance hall, this amplifier has these important factors: reliability, simplicity, flexibility, and ample power. It has a maximum undistorted (0.5%) output of 30 watts. The input for maximum output is 2.5 millivolts.

Simplicity was desirable because unskilled hands were likely to use the equipment. Flexibility was required so that more than one microphone could be used, and provision had to be made for playing phonograph records.

The amplifier has been operating without trouble three hours a night, five nights a week for two years. The power pack, a separate unit, has been in operation for three and one-half years under the same conditions.

Two novel features in the circuit are the tone control stage and the high-gain phase splitter analysed by E. Jeffery in *Wireless World* (London; August, 1947). Thanks are due the latter for considerable personal assistance.

The input circuit is designed for three dynamic microphones and one crystal pickup, and not two of each as shown in the photograph. Simplicity is the keynote and only one microphone transformer is used, a 50/1 Mumetal-shielded type. Mixing is smooth and silent.

## Tone control circuits

The outputs of the microphone transformer and pickup are applied in parallel between grid and ground of the tone control tube, a 6SJ7 (see Fig.1). Variable negative current feedback is applied to this tube by the cathode resistors and associated networks.

The correct value of grid bias is obtained by returning the 220,000-ohm grid resistor to a tap in the cathode circuit.


When the moving contacts of the two tone control potentiometers are grounded, the impedance between cathode and ground is about 5,400 ohms and is independent of frequency; therefore the negative feedback is also independent of frequency and the gain is constant.

When the moving contact of potentiometer R1 is moved to the other end of its track, the network has an impedance which decreases with rise of frequency—3,500 ohms at 1,000 cycles, and 1,300 ohms at 10,000 cycles (see Fig. 2). The corresponding decrease in the negative feedback with increasing frequency causes the gain to rise and the control to act as a treble boost. Fig. 2 also shows the cathode-ground impedance variations with the frequency, with potentiometer R1 at the half-resistance setting.


By similar reasoning, potentiometer

*This rugged and dependable 30-watt amplifier is built for trouble-free operation*

By JAMES RUNDO

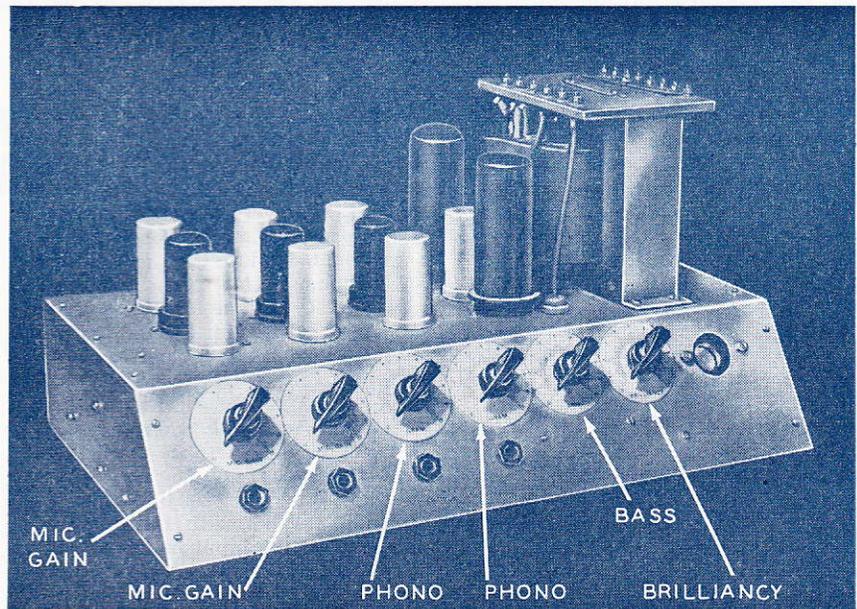

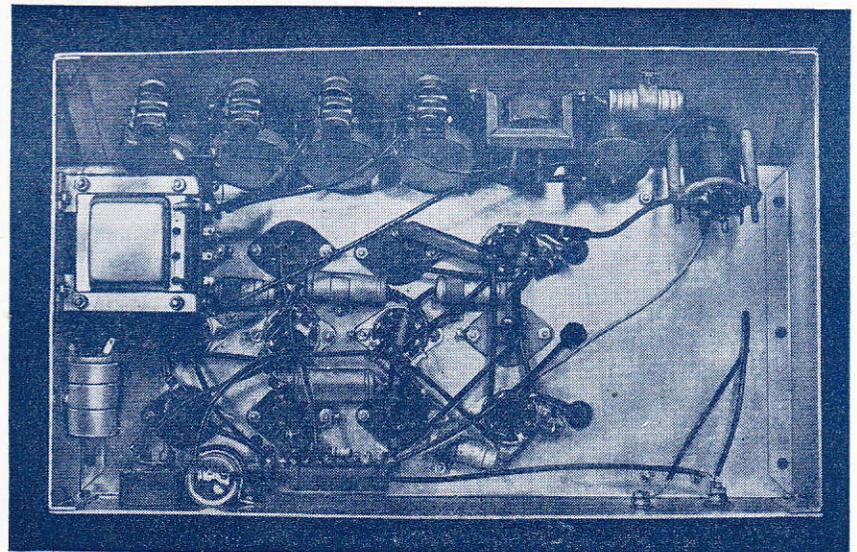Front view of the high-fidelity amplifier. One of the two phono inputs was later changed to a microphone input. All controls are on the sloping panel.



The symmetrical layout under the chassis gives the job a very neat appearance.



electrolytic capacitor after switching off.

As shown in the circuit, an output indicator is included in the amplifier. This consists of a neon lamp, with lim-

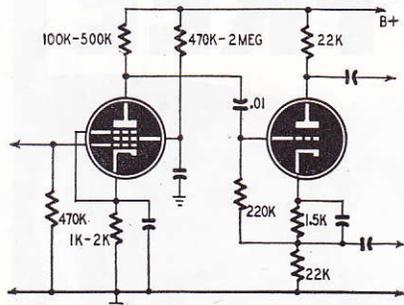


Fig. 4—Conventional cathode follower phase splitter preceded by a pentode.

iting resistors, connected across the primary of the output transformer. The 0.5-watt lamp, a common type of indicator for British standard 230-volt

lines, was uncapped and fitted into the octal base of an old burnt-out tube with Plastic Wood. The values of the limiting resistors were adjusted by trial and error until the indicator is fully lit at 30 watts output.

**Construction hints**

For those readers who contemplate building a similar amplifier, the following constructional notes may be of interest. The chassis of both units are of .064-inch aluminum, and the two chassis measure 15 x 7 x 3 inches and 8 x 6½ x 1½ inches, respectively. The amplifier control panel is set at an angle and the six controls are grouped in a horizontal row, the four input jacks being placed below their respective mixer potentiometers. This, together with a symmetrical layout of the tubes and electrolytic capacitors, gives a neat appearance to the job. Power is carried to the amplifier by a heavy-duty four-wire cable terminated

in a female four-point connector. The speaker output is taken from two insulated binding posts at the rear of the chassis.

While the general layout is not very critical, some precautions must be taken to keep the hum at the lowest possible level because of the amplifier's high gain. One good way to keep hum down is to make all the common ground connections to a single bus bar, then ground the bus bar to the chassis at one point only. This point should be at the input stages or where the signal level is lowest. The heater circuits should be wired with a pair of twisted wires. Do not ground one side of the heaters in the amplifier chassis. The power supply schematic shows one side of the 6.3-volt winding grounded. It is better to ground the centertap of this winding if there is one.

# Preamp for Low-Speed Pickups

By ROBERT HILL


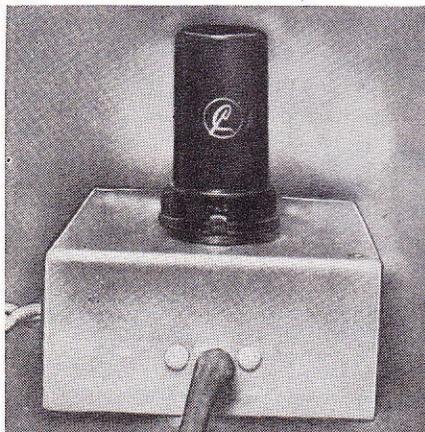


Photo of the tone-compensated preamp.

MANY LP and 45-r.p.m. record players have a low output crystal cartridge which does not give enough output voltage for some radios. Here is a compact preamplifier and tone compensating circuit which will give the needed gain and also provide bass and treble boost.

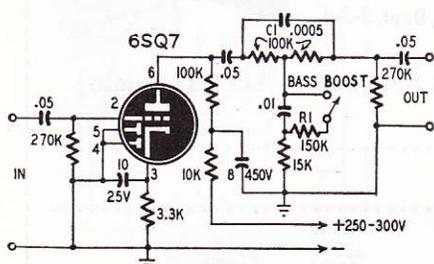The filament and B-plus voltages are obtained from the receiver. If the radio is an old one with 2.5-volt heaters, a type 2A6 tube may be used. A 6AT6 can be used instead of the 6SQ7 if min-




Circuit of the one-tube preamplifier.

ature types are preferred. It is not advisable to use the preamplifier with an a.c.-d.c. set because of the filament connections.

The amplifier output is fed directly to the tone compensating network. For less-high-frequency response, capacitor C1 can be made smaller. An s.p.s.t. switch in series with R1 cuts the bass boost when it is closed. If the bass cut is not great enough, the resistor can be made smaller.

If the 250-300-volt plate supply is not available from the receiver, a lower voltage can be used but the gain of the preamplifier will be lower. In this case it might be advisable to use a duotriode such as the 6SN7 to get additional gain. Use one section of the dual tube as shown in the circuit, and feed the output to the grid of the other section which is hooked up as a straight resistance-coupled amplifier to supply the required gain. Even higher gain can be supplied by using a high-mu duo-triode like the 6SL7.

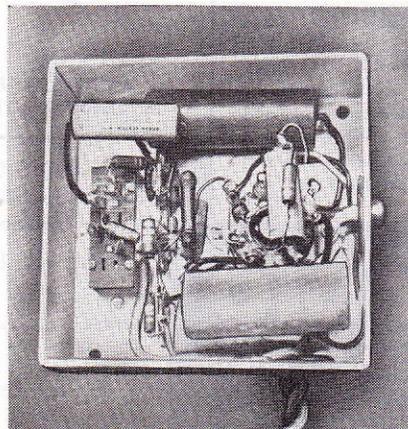

An under-the-chassis photo of the unit.

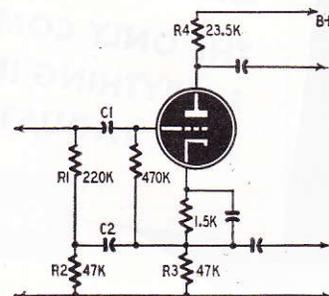


Fig. 5—Re-arrangement of the phase splitter of Fig. 4 for higher gain.

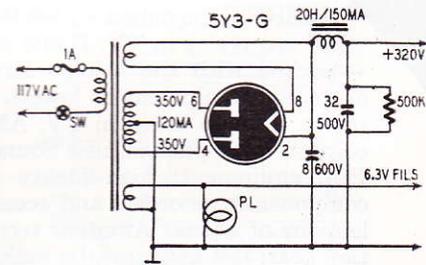


Fig. 6—Power supply for the amplifier.

The photographs show the placement of parts, which is not very critical. All resistors and capacitors have 20% tolerance. The common bias resistor of the 6L6 output tubes largely compensates for any slight mismatch of the resistors in the phase splitter circuit. The 23,500-ohm resistor may be 22,000- and 1,500-ohm units in series. The two 50-µf electrolytic capacitors are mounted with their cans isolated from ground. All coupling, decoupling, and smoothing capacitors are rated at least 500 volts, as the B-supply reaches this value before the output tubes are fully conducting.

**RESPONSE TABLE**

Frequency (cycles)	Min. Treble Min. Bass (response) (db)	Max. Treble Min. Bass (db)	Min. Treble Max. Bass (db)
40	-0.5	0	+10.2
100		+0.1	+8.6
200	0	+0.3	+6.6
400	0	+0.8	+4.2
1,000	0	+3.2	+1.3
2,000	0	+5.7	+0.4
4,000	0	+8.0	+0.1
10,000	0	+9.9	0
15,000	+1.0	+11.3	+1.0
20,000	0	+10.6	0
40,000	-0.7	+10.3	-0.7